
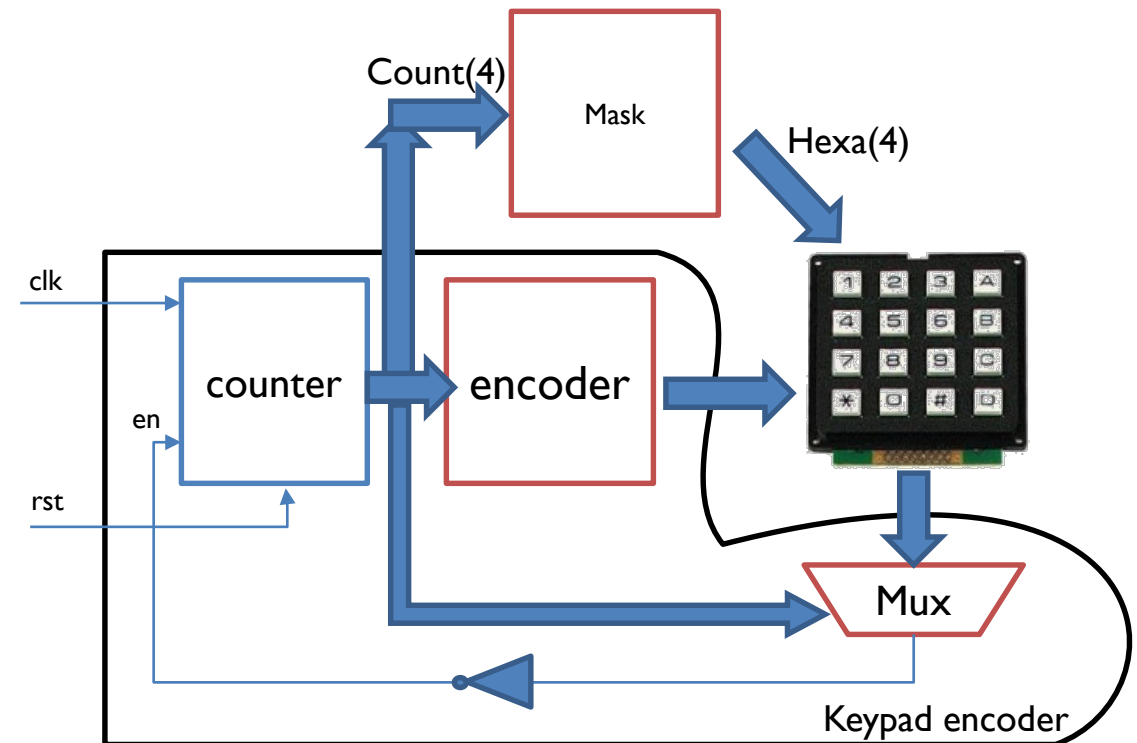


Lecture 3: Registers and FSMs

By: Emad Samuel Malki Ebeid


Summary of lecture 2

 

Look to the blackboard notes

- Latches & Flip flops
- Parallel & shift registers
- FSMs
 - debouncer


Moore State Machine

 

The outputs of a Moore state machine depend **only on the present state**. The outputs are written **only** when the state changes (on the clock edge).

FSM

Mealy State Machine

 


The outputs of a Mealy state machine depend on **both the inputs and the current state**. When the inputs change, the outputs are updated **without** waiting for a clock edge.


Because modern designs are generally synchronous, the **Moore** option tends to be preferred – *Finite State Machine in Hardware* book by Volnei A. Pedroni

FSM in hardware

Moore

 

Mealy

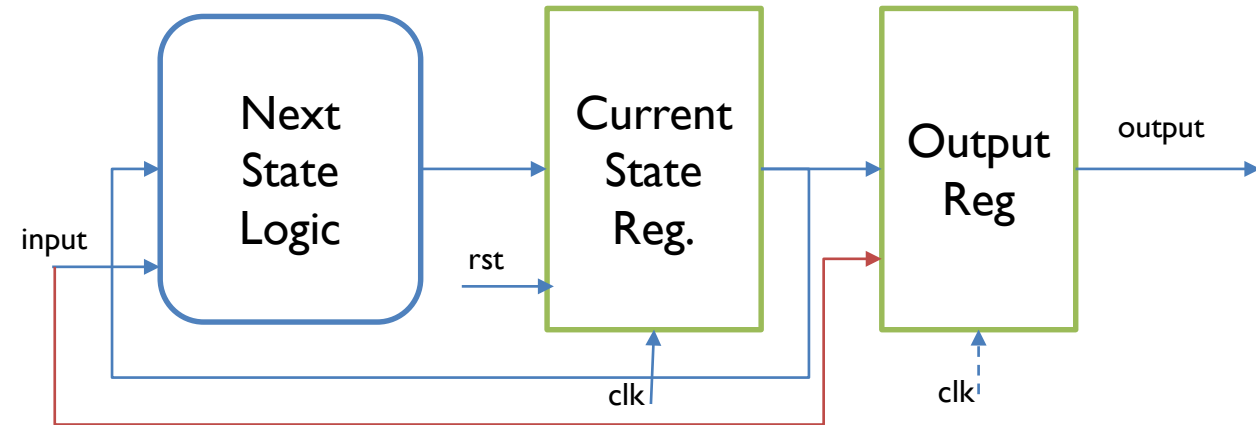

FSM examples: debouncer

```

ENTITY fsm_intr IS
PORT (
    clk      : IN      std_logic;
    rst      : IN      std_logic;
    strobe   : IN      std_logic;
    intr     : OUT     std_logic
);

-- Declarations

END fsm_intr ;

```

```



ARCHITECTURE fsm OF fsm_intr IS



-- Architecture Declarations
TYPE STATE_TYPE IS (s0, s1, s2); -- Define the states

-- Declare current and next state signals
SIGNAL current_state : STATE_TYPE ; -- Create a signal that uses the different states
SIGNAL next_state : STATE_TYPE ;

BEGIN

```

  

  

```

clocked : PROCESS (clk, rst)
BEGIN
  IF (rst = '1') THEN
    current_state <= s0;
    -- Reset Values
  ELSIF (rising_edge(clk)) THEN
    current_state <= next_state;
    -- Default Assignment To Internals

    -- Combined Actions for internal signals only
    -- CASE current_state IS
    -- WHEN s0 =>
    --   reg<= data_in & '1';
    -- WHEN s2 =>
    --   count<= count +1;
    -- WHEN OTHERS =>
    --   NULL;
    -- END CASE;
  END IF;
END PROCESS clocked;

```

```

nextstate : PROCESS (current_state, strobe)
BEGIN
  CASE current_state IS
    WHEN s0 =>
      IF (strobe = '1') THEN
        next_state <= s1;
      ELSE
        next_state <= s0;
      END IF;
    WHEN s1 =>
      next_state <= s2;
    WHEN s2 =>
      IF (strobe = '0') THEN --IF (count = 10) THEN
        next_state <= s0;
      ELSE
        next_state <= s2;
      END IF;
    WHEN OTHERS =>
      next_state <= s0;
  END CASE;
END PROCESS nextstate;

```

```

output : PROCESS (current_state)
BEGIN
  -- Default Assignment
  intr <= '0';
  -- Default Assignment To Internals


  -- Combined Actions
  CASE current_state IS
    WHEN s0 =>
      intr <= '0';
    WHEN s1 =>
      intr <= '1';
    WHEN s2 =>
      intr <= '0';
    WHEN OTHERS =>
      NULL;
  END CASE;

  END PROCESS output;

  -- Concurrent Statements


END fsm;

```

 

Lab3: FPGA configuration

- Design a circuit in VHDL to display a pressed key from the provided 4x4 keypad.
 - Use FPGA LEDs to display the pressed key.
 - Simulate the overall circuit when number **3** is pressed (0011).
 - Configure the final design on the FPGA.

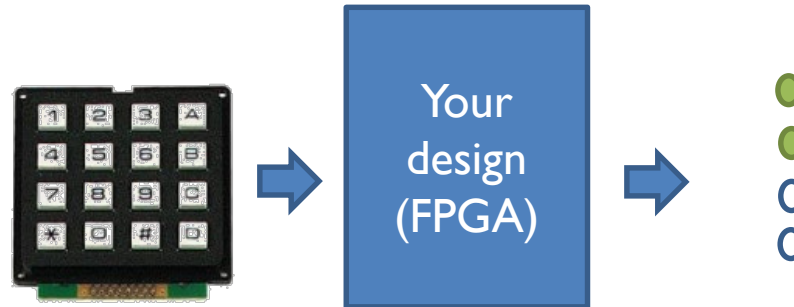

Journal I – delivery 27/09/2020 23:59

- Implement the keypad circuit in FPGA to display a constant pressed key (0011)
 - Use 7-segment display to display the pressed key. You can get one from the component lab (remember to add current limiting resistors (220Ω) as shown in the figure))
 - Use debouncer to avoid the bouncing effect of the contact (push button) before reaching the stable state.
 - The report should include the overall design (Vivado snapshot), simulation results and a photo of the final implementation. Comment on the results.



Key pressed

Your design
(FPGA)

