
 
 
 


# **Lecture 2: FPGA fabric, memories and high-level synthesis**


Emad Samuel Malki Ebeid
 
# Summary of lecture I

- Transistor revolution
- IC issues
  - Power dissipation
  - Power distribution
  - Clock distribution
  - Noise
  - etc.




 
$$\text{Clock Frequency} = \frac{1}{2 * t_p * N}$$


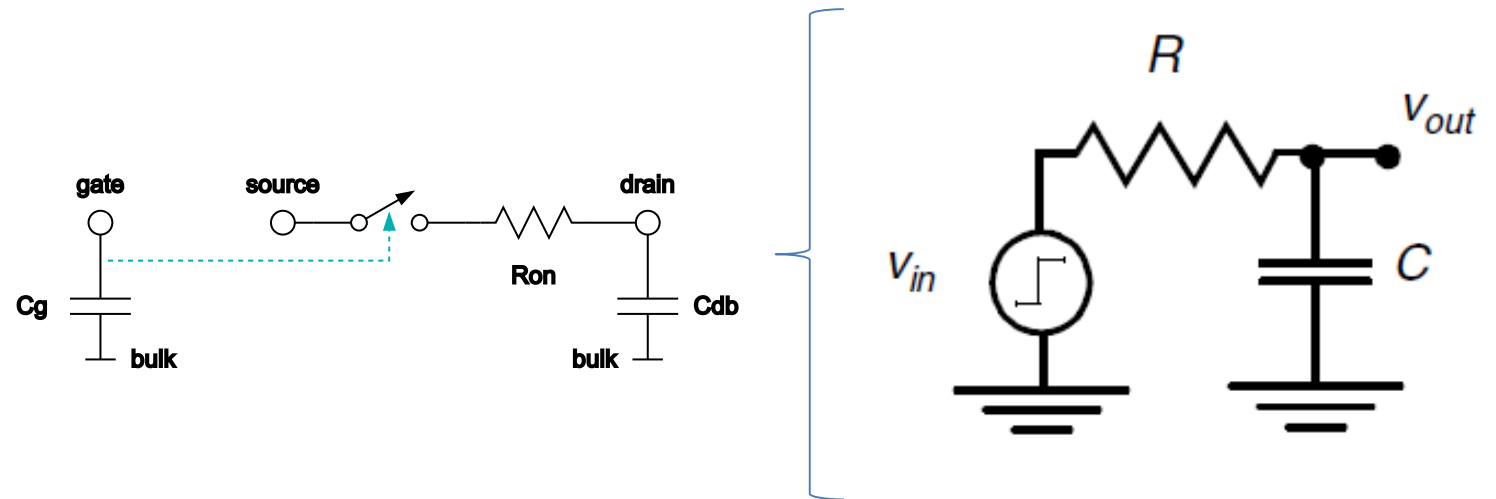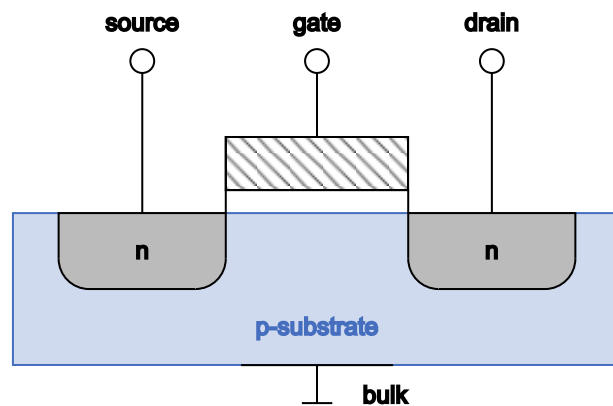
## Propagation delay of the first-order $RC$ networks

- The  $RC$  step response is a fundamental behavior of all digital circuits and thus digital circuits are often modeled as first-order  $RC$  networks.
- The propagation delay of the circuit is of considerable interest.




# Propagation delay

## First order RC network

- $V_{in} = R * i(t) + v_{out}(t)$
- $v_{out}(t) = v_c(t) = \frac{1}{C} \int_0^t i(t) dt$
- Hence,  $V_{in} = R * i(t) + \frac{1}{C} \int_0^t i(t) dt$

To calculate  $i(t)$ , take the derivative

 - $0 = R \frac{di(t)}{dt} + \frac{1}{C} i(t) \Rightarrow \frac{di(t)}{dt} + \frac{1}{RC} i(t) = 0$  (solve the diff. Equations)
- $i(t) = I_0 e^{-\frac{t}{RC}}$  & when  $t = 0, I_0 = \frac{V_{in}}{R}$
- $v_{out}(t) = \frac{1}{C} \int_0^t \frac{V_{in}}{R} e^{-\frac{t}{RC}} dt = V_{in} (1 - e^{-\frac{t}{RC}}) = V_{in} (1 - e^{-\frac{t}{\tau}})$  where  $\tau = RC$  (time constant)





# Propagation delay

## First order RC network (another solution)

$$\begin{aligned}
 V_{out} &= V_{in} \frac{X_c}{R + X_c} \stackrel{s \text{ domain}}{=} \frac{1}{s} \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{s} \cdot \frac{1}{sRC + 1} \\
 &= \frac{A}{s} + \frac{B}{sRC + 1} \quad \Leftarrow \text{Partial fraction} \\
 A \Big|_{s=0} &= 1 & B \Big|_{s=-\frac{1}{RC}} &= -RC \\
 &= \frac{1}{s} + \frac{-RC}{sRC + 1} = \frac{1}{s} - \frac{1}{s + \frac{1}{RC}} \\
 V_{out} &= (1 - e^{-\frac{t}{RC}}) V_{in}
 \end{aligned}$$

Laplace transform:-

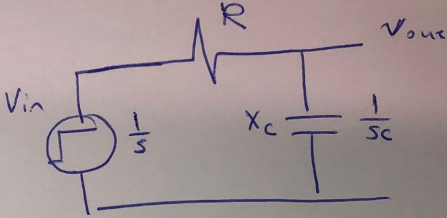 
$$\begin{aligned}
 U(s) &= \frac{1}{s} \\
 e^{-\alpha t} U(t) &= \frac{1}{s + \alpha}
 \end{aligned}$$




# Power and Energy Consumption

- It determines how much energy is consumed per operation and heat the circuit dissipates.
- Design decisions depends on:
  - power-supply capacity
  - battery lifetime
  - supply-line
  - sizing
  - packaging
  - cooling

# Power and Energy Consumption

 

- Dissipation measures:


$$P_{peak} = i_{peak} V_{supply} = \max[p(t)]$$

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{supply}}{T} \int_0^T i_{supply}(t) dt$$


Where:

- $p(t)$  is the instantaneous power
- $i_{supply}$  is current being drawn from the supply voltage  $V_{supply}$
- *higher the number of switching events, the higher the dynamic power consumption.*

 *PDP (power-delay product): energy consumed by the gate per switching event*


 
# Energy Dissipation of First-Order RC Network



- Total energy delivered by the source

$$E_{in} = \int_0^{\infty} i_{in}(t) v_{in}(t) dt = V \int_0^{\infty} C \frac{dv_{out}}{dt} dt = (CV) \int_0^V dv_{out} = CV^2$$

- Energy stored in the capacitor

$$E_C = \int_0^{\infty} i_C(t) v_{out}(t) dt = \int_0^{\infty} C \frac{dv_{out}}{dt} v_{out} dt = C \int_0^V v_{out} dv_{out} = \frac{CV^2}{2}$$



- Where is the other half?




# MOSFETs
  
# MOSFET


- The metal-oxide-semiconductor field-effect transistor (MOSFET or MOS, for short).
- Its major asset from a digital perspective is that the device performs very well as a **switch**




(a) NMOS transistor as 4-terminal device

 

(b) NMOS transistor as 3-terminal device

 



(a) PMOS transistor as 4-terminal device

 

(d) PMOS transistor as 3-terminal device

 
 
# Types

- N-MOS & P-MOS
  - Enhancement-mode MOSFET is off at zero gate–source voltage (no channel).
  - Depletion-mode MOSFET, is normally *ON* at zero gate–source voltage (channel).



  
# The Threshold Voltage

- Cut off region
  - $V_{GS} = 0$
- Linear region (ohmic region)
  - $V_{GS} > V_T$
  - $V_{DS} < V_{GS} - V_T$
- Saturation region
  - $V_{GS} > V_T$
  - $V_{DS} > V_{GS} - V_T$




# Semiconductor manufacturing process

 

<https://www.youtube.com/watch?v=Q5paWn7bFg4>


# Semiconductor manufacturing process

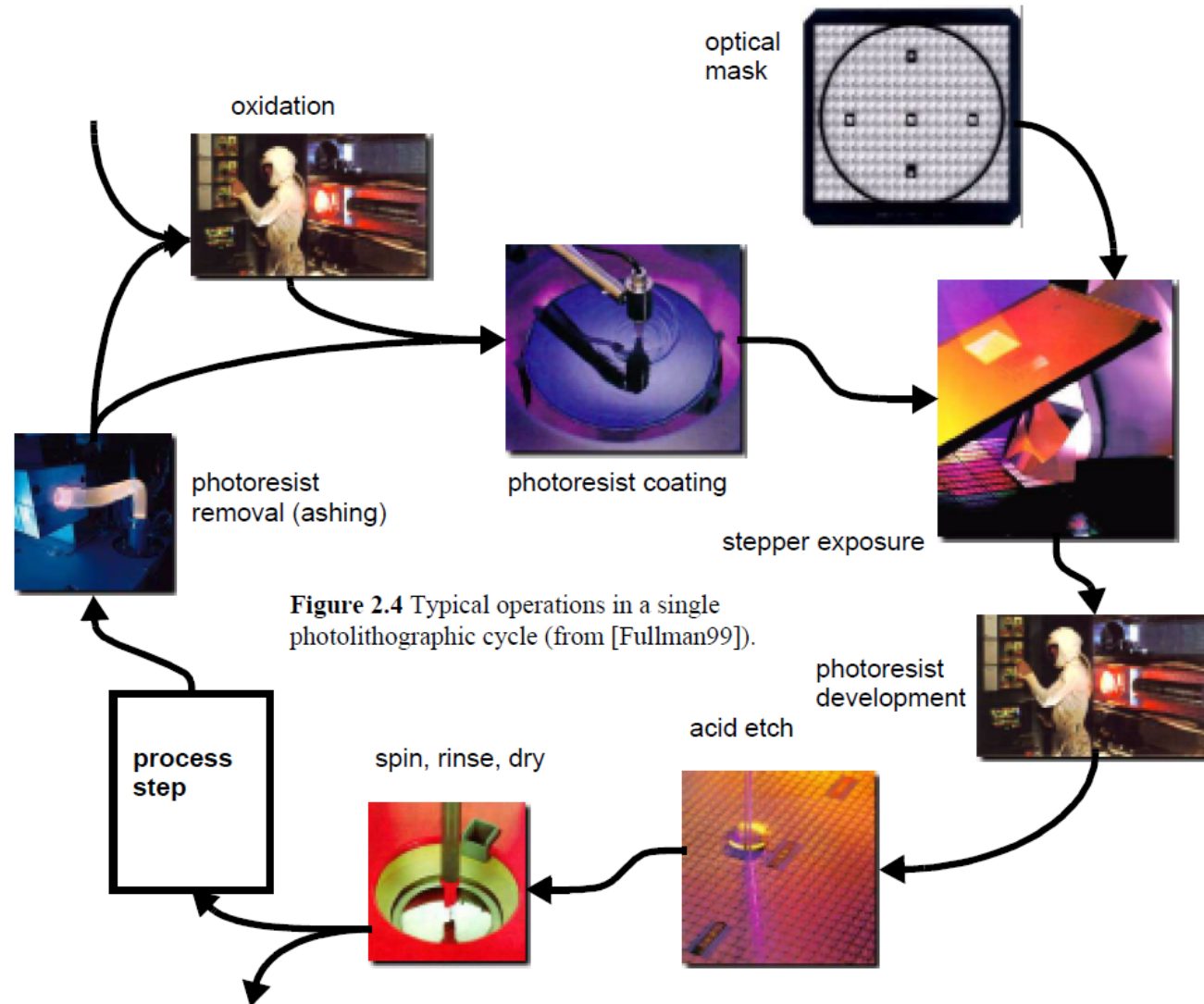

**Figure 2.4** Typical operations in a single photolithographic cycle (from [Fullman99]).


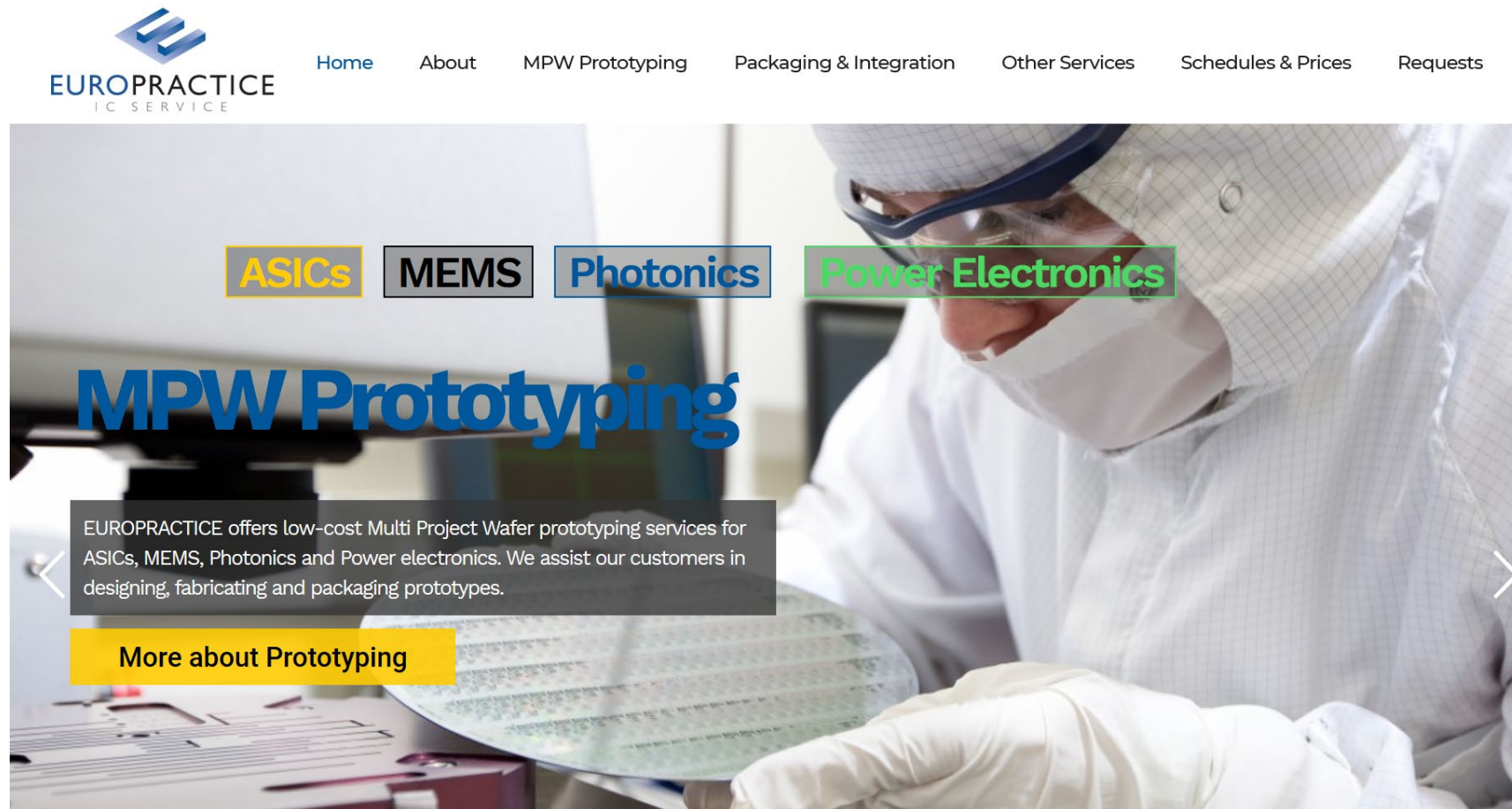
# Build "your" IC

- <http://europpractice-ic.com/> IC services for research institutes


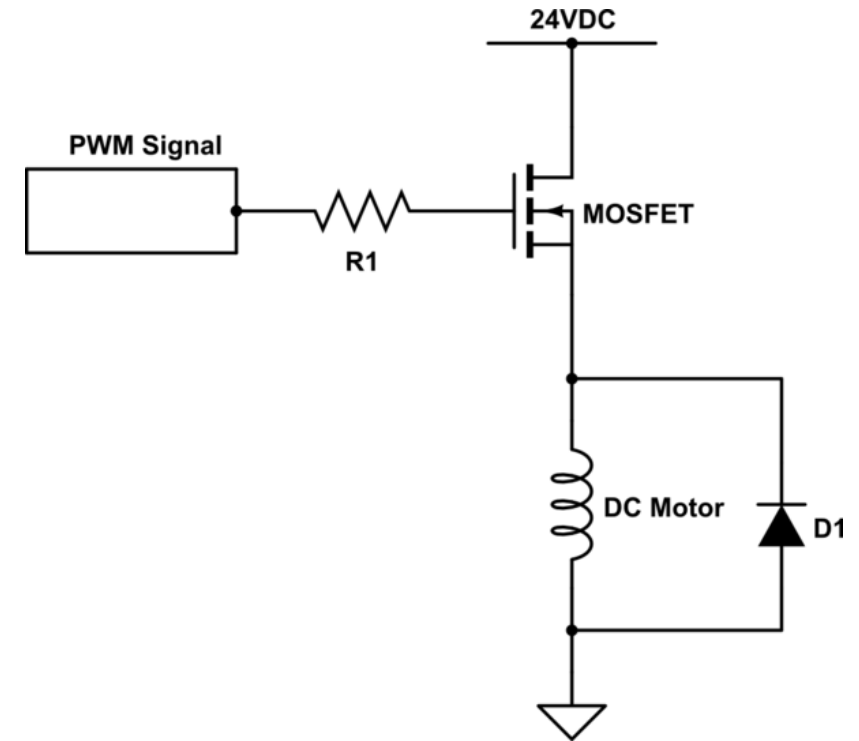 
# Applications


- DC motor drive
- DC relay
- Inverter
- Amplifier
- passive element
  - resistor, capacitor and inductor
- digital circuit






# Logic gates

- Inverter

 


- NOR

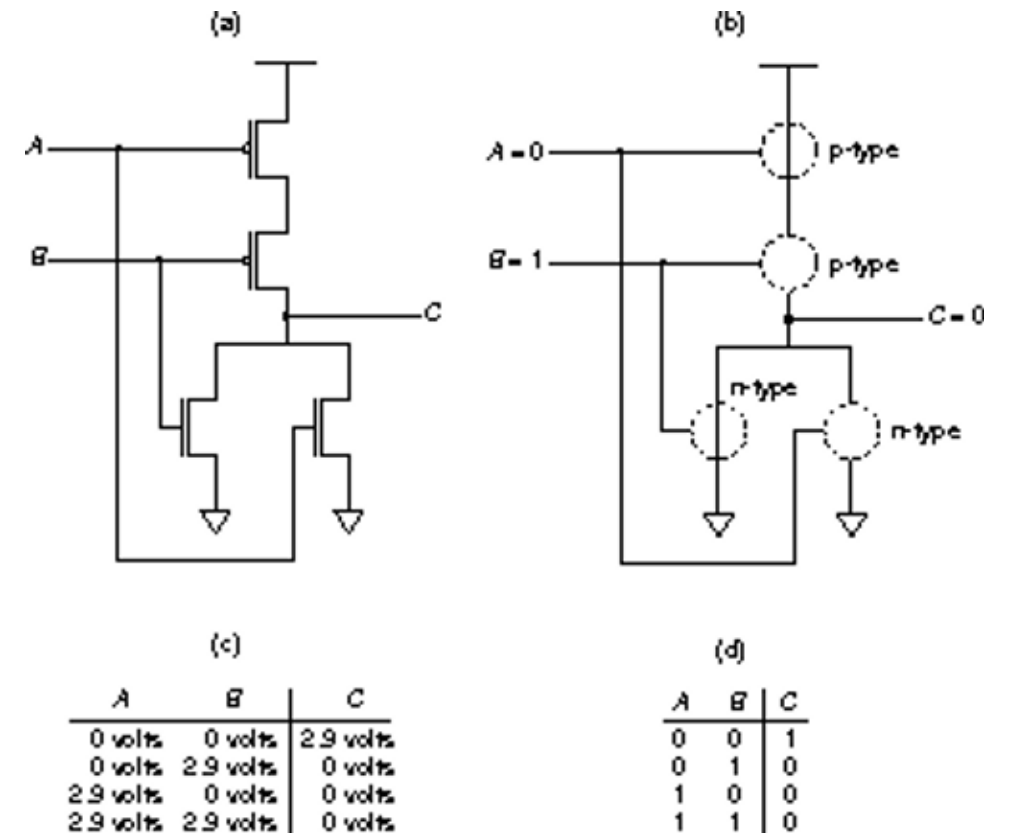

# Logic gates

- AND


(10 minutes)

 

(b)

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

- OR

 


(c)

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 |

 
# Multiplexer

- Its function is to select one of the inputs and connect it to the output




Draw the logic diagram  
(5 minutes)

# Look-up tables (LUT)

 

# LUT of logic gates

- AND
- OR
- Invert
- XOR


 


# FPGA

- Field Programmable Gate Array (FPGA) is an integrated circuit containing gate matrix which can be programmed by the user “in the field” without using expensive equipment.
- An FPGA contains a set of programmable logic gates and rich interconnect resources, making it possible to implement complex digital circuits.
- FPGA devices are produced by a number of semiconductor companies:
  - Xilinx, Altera, Actel, Lattice, QuickLogic and Atmel.
- Configuration bitstream can be stored in FPGA using various technologies.
  - The majority of FPGAs is based on SRAM (Static RAM).
 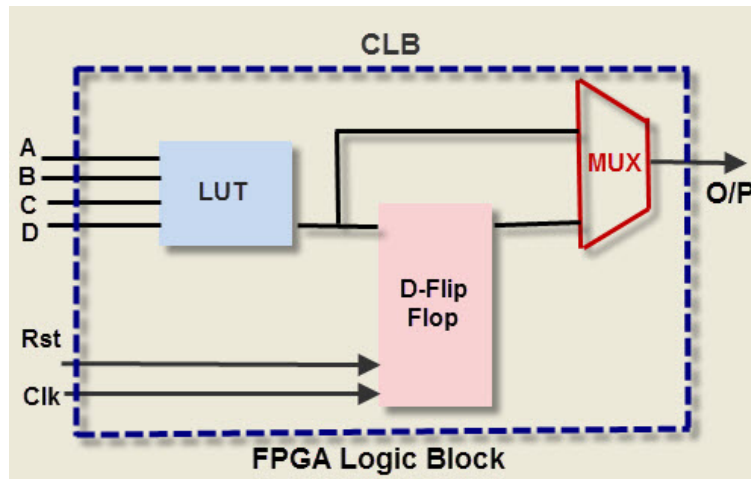
# FPGA

- Field Programmable Gate Array
- The general FPGA architecture consists of three types of modules. They are I/O blocks or Pads, Switch Matrix/ Interconnection Wires and Configurable logic blocks (CLB).




# Memory cells: RAM

RAM is a **volatile** memory that the data is eventually lost when the memory is not powered



 
## SRAM: Static random-access memory

- Speed  $\uparrow$  size (bigger)
- Cache memory
- Low power consumption


 
## DRAM: Dynamic random-access memory

- Speed  $\downarrow$  size (smaller)
- Main memory
- Charge leakage
- High power consumption
- Refreshed frequently (few milliseconds)



Single Memory Cell





# SRAM-based FPGAs

- It stores logic cells configuration data in the static memory
- Since SRAM is volatile, the FPGAs must be programmed (configured) upon start
- There are two basic modes of programming:
  - **Master mode**, when FPGA reads configuration data from an external source, such as an external Flash memory chip.
  - **Slave mode**, when FPGA is configured by an external master device, such as a processor (via a dedicated configuration interface or via a boundary-scan (JTAG) interface).
- SRAM-based FPGAs with an internal flash memory:
  - it contains internal flash memory blocks, thus eliminating the need to have an external non-volatile memory. It uses flash only during startup to load data to the SRAM configuration cells.
  
# Programmable switch FPGAs

- It uses flash as a primary resource for configuration storage, and doesn't require SRAM
- Switch is a floating-gate transistor that can be turned off by injecting charge onto its floating gate
- It has a limit number of reprogramming
- More secure than SRAM-FPGA





# Fuse-based FPGA


- One time program (OTP) FPGA
- The fuse makes or breaks link between two wires
- More secure than SRAM (no load from an external device )
- In high radiation environments (space or nuclear reactors), radiation events can cause SRAM, that contains the program, to change state but not in fused FPGA.
  
# Programmable switch matrix

- All internal connections are composed of metal segments with programmable switching points and switching matrices to implement the desired routing.



# Example: FPGA programming

 

$$f_1 = x_1 x_2$$

$$f_2 = \overline{x_2} x_3$$

$$f = x_1 x_2 + \overline{x_2} x_3$$

## Other FPGA Building Blocks

- Clock distribution: element clock skew
- Embedded memory blocks
- Special purpose blocks:
  - DSP blocks: Hardware multipliers, adders and registers
  - Embedded microprocessors/microcontrollers
  - High-speed serial transceivers

# Design flow

Design and implement a simple unit permitting to speed up encryption with RC5-similar cipher with fixed key set on 80331 microcontroller. Unlike in the experiment 5, this time your unit has to be able to perform an encryption algorithm by itself, executing 32 rounds.....



Specification / Pseudocode

On-paper hardware design




```
Library IEEE;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity RC5_core is
    port(
        clock, reset, over_done: in std_logic;
        data_input: in std_logic_vector(7 downto 0);
        data_output: out std_logic_vector(7 downto 0);
        out_full: in std_logic;
        key_input: in std_logic_vector(31 downto 0);
        key_read: out std_logic;
        k: out AFS_core;
    end RC5_core;
```




Synthesis

 


Functional simulation

 


Post-synthesis simulation

 

Implementation

 


Timing simulation

 

Configuration



On chip testing


 


# Synthesis

```
architecture MLU_DATAFLOW of MLU is
  signal A1:STD_LOGIC;
  signal B1:STD_LOGIC;
  signal Y1:STD_LOGIC;
  signal MUX_0, MUX_1, MUX_2, MUX_3: STD_LOGIC;
begin
  A1<=A when (NEG_A='0') else
    not A;
  B1<=B when (NEG_B='0') else
    not B;
  Y<=Y1 when (NEG_Y='0') else
    not Y1;

  MUX_0<=A1 and B1;
  MUX_1<=A1 or B1;
  MUX_2<=A1 xor B1;
  MUX_3<=A1 xnor B1;

    with (L1 & L0) select
    Y1<=MUX_0 when "00",
        MUX_1 when "01",
        MUX_2 when "10",
        MUX_3 when others;
end MLU_DATAFLOW;
```




Mapping


Circuit netlist



# Placing

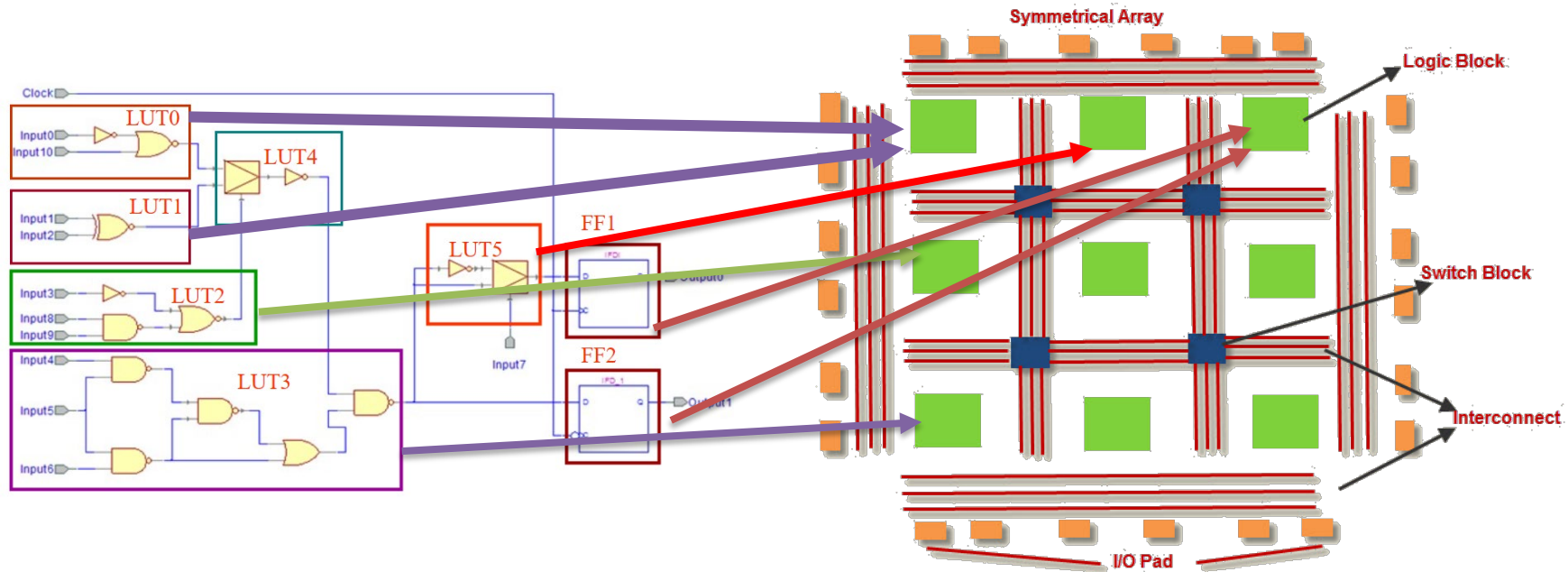


# Routing

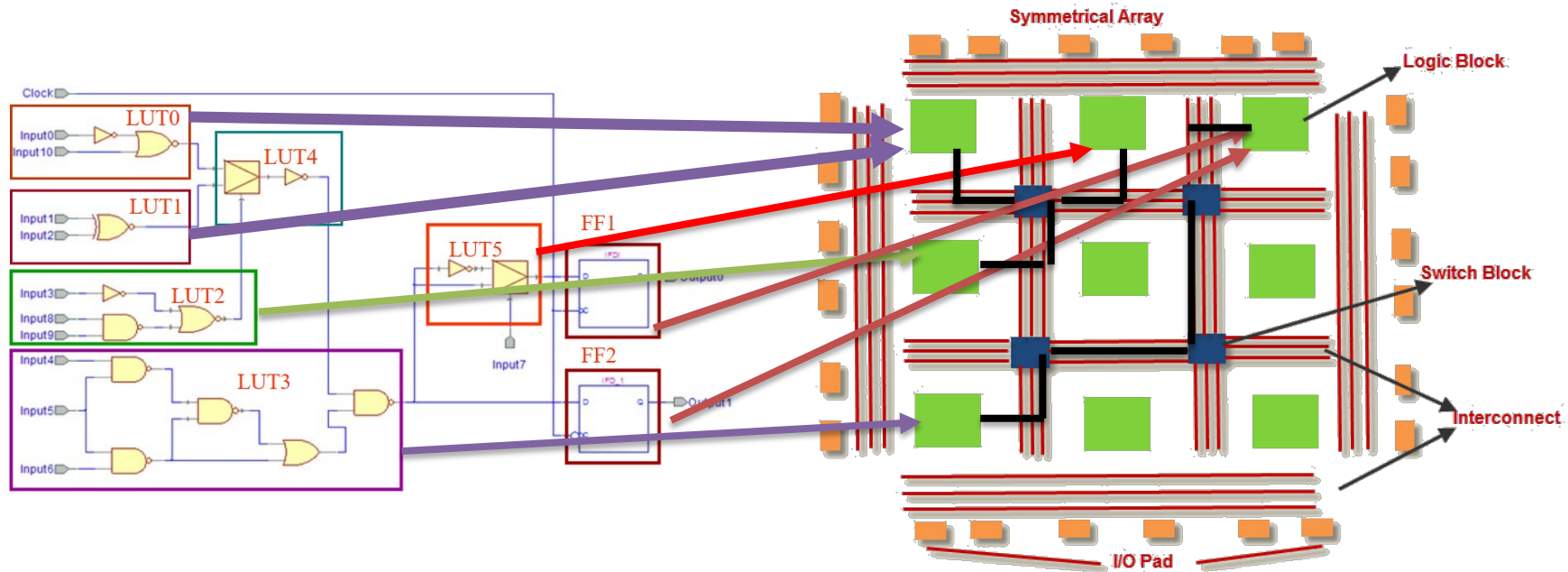

# Configuration

- Once a design is implemented, the synthesis tool generates a file that the FPGA can understand
- This file is called a bit stream: a BIT file (.bit extension)
- The BIT file can be downloaded directly to the FPGA, or can be converted into a PROM file which stores the programming information

**Look to the black board notes**

 

# Functional simulation

- Build the follows
  - Inverter
  - Dec 2-4
  - Mux 4-1
  - 4 bit Counter
- Build keypad interface
  - Block design
    - Connect buses
    - Connect keypad module